

Verilog HDL语言

Verilog程序设计方法


主讲：卢 萍

华中科技大学计算机科学与技术学院

Module Styles

- Modules can be specified different ways
 - **Structural** – connect primitives and modules
 - **Dataflow** – use **assign** continuous assignments
assign <LHS net> = <RHS expression>;
 - **Behavioral** – use **initial** and **always** blocks
- A single module can use more than one method!
- What are the differences?

Full Adder: Structural

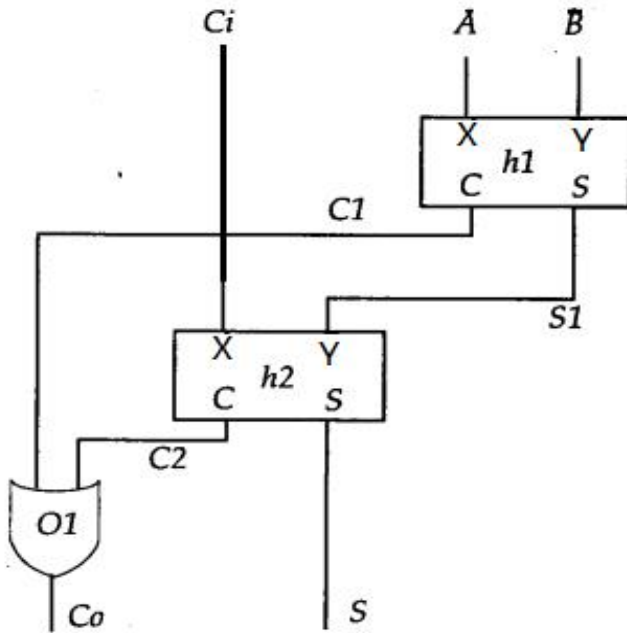

```
module half_add (X, Y, S, C);
```

```
input X, Y ;
```

```
output S, C ;
```

```
xor SUM (S, X, Y); // 异或门实例语句  
and CARRY (C, X, Y); // 与门实例语句
```

```
endmodule
```

使用两个半加器模块构造全加器

```
module full_add ( input A, B, CI, output S, CO) ;
```

```
wire S1, C1, C2;
```

```
half_add h1 (A, B, S1, C1),
```

```
           h2 (S1, CI, S, C2); //两个 半加器模块实例语句
```

```
or CARRY (CO, C2, C1); // 或门实例语句
```

```
endmodule
```

Full Adder: Dataflow

```
module fa_rtl (A, B, CI, S, CO) ;  
  
input A, B, CI ;  
output S, CO ;  
  
// use continuous assignments  
assign S = A ^ B ^ CI;  
assign CO = (A & B) | (A & CI) | (B & CI);  
  
endmodule
```

Data flow Verilog is
often very concise
and still easy to read

Works great for most
boolean and even
datapath descriptions


Full Adder: Behavioral

- 只要有事件发生（列表中任何 信号有变化），就执行begin...end 的语句（for simulation）
---- 实际上，列表中信号的改变影响输出

```
module fa_bhv (A, B, CI, S, CO);  
  
input A, B, CI;  
output S, CO;  
reg S, CO;           // 只有reg型能够在 always 语句中被赋值  
  
always@(A or B or CI) // 由事件控制的always语句  
begin  
    S = A ^ B ^ CI;      // 过程性赋值语句,, 必须在 always 过程块中  
    CO = (A & B) | (A & CI) | (B & CI);  
end  
endmodule
```

Mix Styles
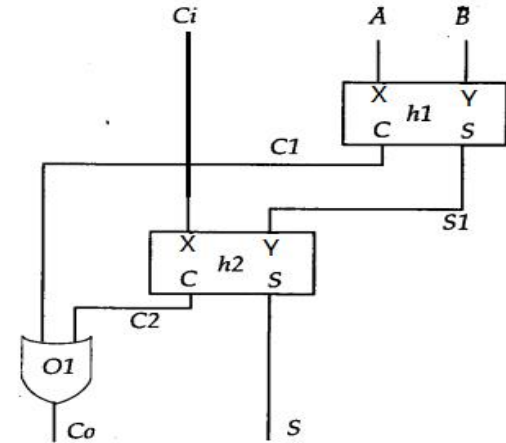
```
module Add_half_bhv(C, S, X, Y);
  output reg S, C;
  input X, Y;
  always @(X, Y) begin
    S = X ^ Y;
    C = X & Y;
  end
endmodule
```



```
module Add_full_mix(CO, S, A, B, Ci) ;
  output S, CO;
  input A, B, Ci;
  wire s1, c1, c2;
  Add_half_bhv h1(.S(s1), .C(C1), .X(A), .Y(B));
  Add_half_bhv h2(.S(S), .C(C2), .X(Ci), .Y(S1));
  assign CO = C1 | C2;
endmodule
```

原语(Primitives)

- 不用声明，直接实例化
- 输出端口在前，输入端口在后
- 实例名和时延可选

and N25(Z, A, B, C); // N25是实例名

and #10 (Z, A, B, X),

(X, C, D, E); // delay specified, 2 gates

and #10 N30 (Z, A, B); // name and delay specified

Syntax For Structural Verilog

```
module full_add ( input A, B, CI, output S, CO );
```

```
    wire S1, C1, C2;
```

```
    half_add h1 (A, B, S1, C1), //实例化两个 half_add半加器子模块
```

```
        h2 (C1, S1, S, C2); // 端口位置关联
```

```
    or CARRY (CO, C2, C1); // 实例化或门原语
```

```
endmodule
```


```
module half_add (X, Y, S, C);
```

```
    input X, Y;
```

```
    output S, C;
```

```
    ....
```

```
endmodule
```

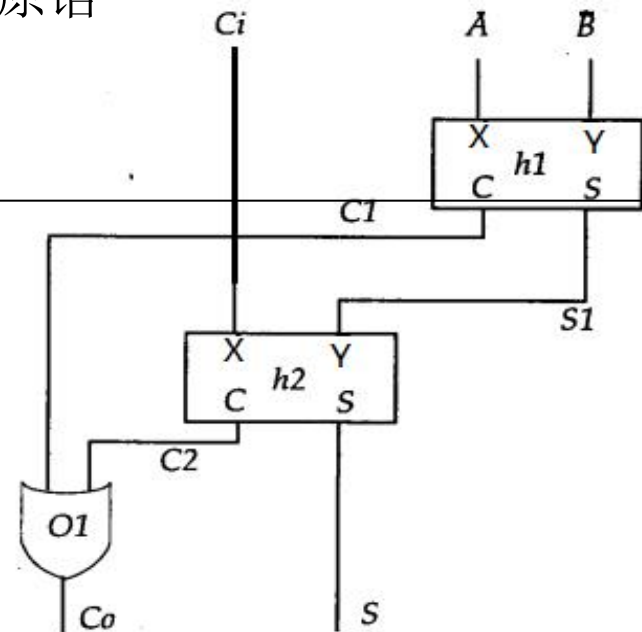

.<port name>(<signal name>)


```
module Add_full(Co,S, A, B, Ci) ;  
  output Co,S;  
  input A, B, Ci;  
  wire S1, C1, C2;
```

```
  Add_half h1( .C(C1), .S(S1), .X(A), .Y(B)); /* 端口名称关联 */
```

```
  Add_half h2( .C(C2), .S(S), .X(Ci), .Y(S1));
```

```
  or carry_bit(Co, C1, C2); /* 端口位置关联 */
```

```
endmodule
```

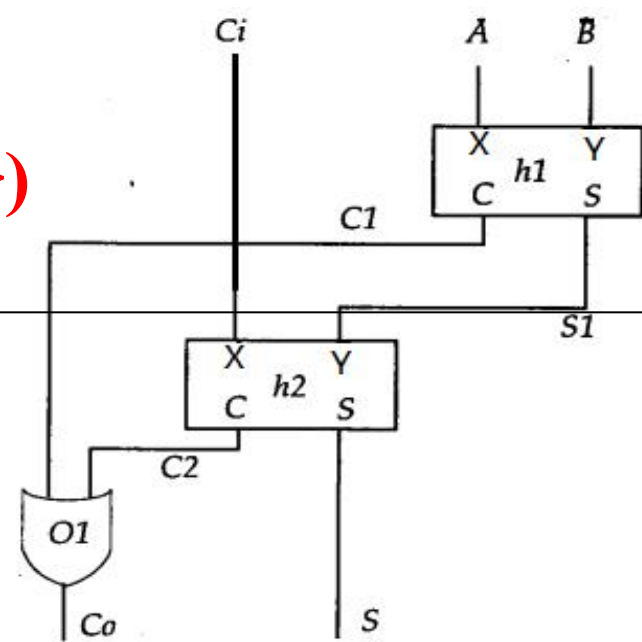

```
module half_add (X, Y, S, C);  
  input X, Y ;  
  output S, C ;  
  ....  
endmodule
```

Empty Port Connections

- Example: **module** Add_full(Co,S, A, B, Ci) ;
 - Add_full AF(Cout,Sum, a, , cin) ; // B is high impedance (z)
 - Add_full AF(,Sum, a, b , cin) ; // Outputs Co unused.
- General rules
 - Empty input ports => high impedance state (z)
 - Empty output ports => output not used
- Specify all input ports anyway!
 - Z as an input is very bad...why?
- Helps if no connection to output port name but leave empty:
 - Add_full AF(.Co()),.S(Sum),.A(a),.b(B) , .Ci(cin)) ;

```

module Add4bit(cout, s, a, b);
  output [3:0] s;
  output cout;
  input [3:0] a, b;
  wire cout0, cout1, cout2; // 内部信号
  Add_full A0(cout0, s[0], a[0], b[0], 1'b0);
  Add_full A1(cout1, s[1], a[1], b[1], cout0);
  Add_full A2(cout2, s[2], a[2], b[2], cout1);
  Add_full A3(cout, s[3], a[3], b[3], cout2);
endmodule

```


Example:
Detecting cout2

Must output
cout2


```

module Add_full (Co,S, A, B, Ci);
  input A, B, Ci ;
  output S, Co ;
  ....
endmodule

```

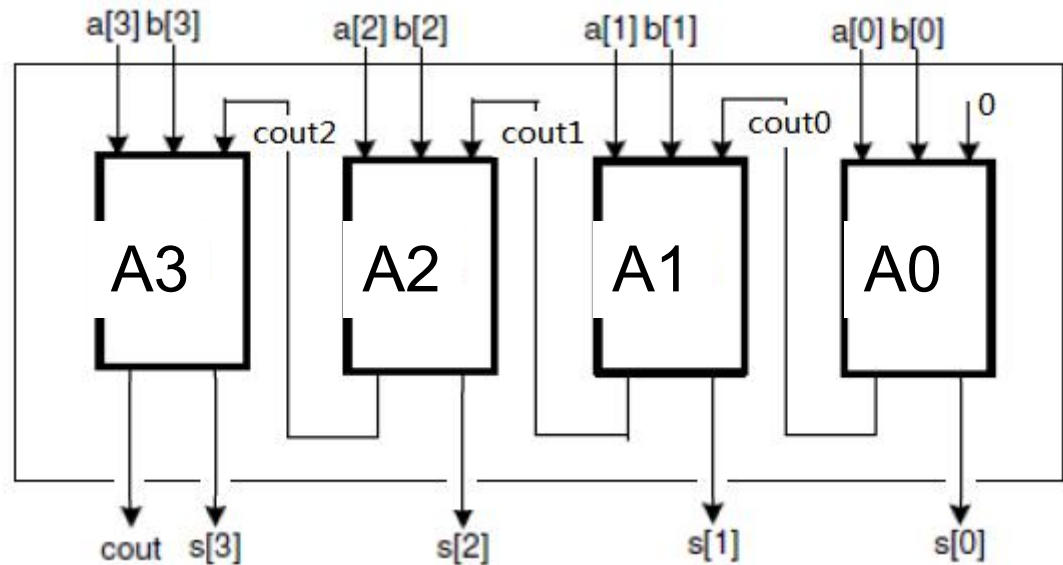



层次结构

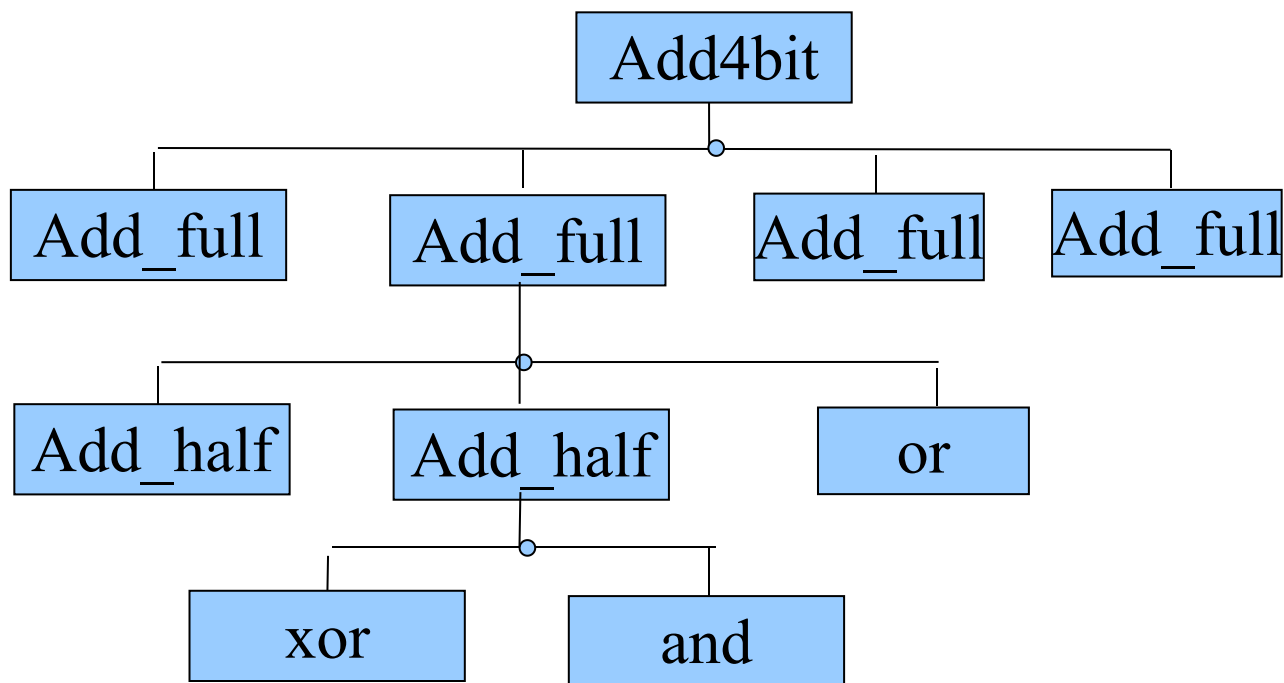

4位加法器的层次结构

层次化 与 源文件

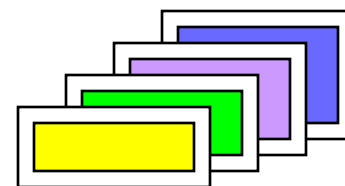 - 多个module是放在同一个文件还是分开放?
- 可以放在同一个文件中
 - 模块次序自由
 - 适合于小设计
 - 不太适合模块重用（剪切和粘贴）
- 可以将模块分解成多个文件
 - 良好习惯：每个文件只包含一个module
 - 有助于组织模块
 - 便于找到一个模块
 - 有利于模块重用（将文件添加到项目中）




Dataflow Verilog

- The continuous assign statement
 - It is the main construct of Dataflow Verilog
 - It is **deceptively** powerful & useful
- More basic generic form:
`assign [delay] <LHS_net> = <RHS_expression>;`
- If RHS (right hand side) result changes, LHS is updated with new value
 - Constantly operating (“continuous”)
 - It's *hardware!*

Back to the Continuous Assign

- RHS can use operators (i.e. $+$, $-$, $\&$, $|$, $^$, \sim , $>>$, ...)

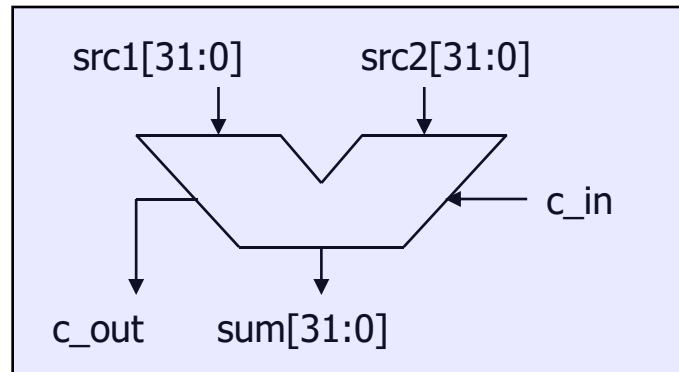

```
wire [31:0] sum, src1, src2;  
wire c_in, c_out;  
assign {c_out, sum} = src1 + src2 + c_in;
```

□ Verilog运算符（9类）

- 算术运算符：+、-、*、/、%
- 位运算符：~、&、|、^、 $\wedge\sim$ 或 $\sim\wedge$ （异或非）
- 缩位运算符（单目）：&、~&(与非)、|、~|、^、 $\wedge\sim$ 、 $\sim\wedge$
- 逻辑运算符：!、&&、||
- 关系运算符（双目）：<、>、<=、>=
- 相等与全等运算符： $\mathbf{==}$ （逻辑相等）、 $\mathbf{!=}$ （逻辑不等）、 $\mathbf{===}$ （全等）、 $\mathbf{!==}$ （非全等）
- 逻辑移位运算符：<<、>>
- 连接运算符：{ }
- 条件运算符：?:

Behavioral Verilog

- 行为建模的主要机制： **initial** and **always**
 - 所有其他的行为语句包含在这两个语句中
 - **initial** and **always** 块不能嵌套
 - 左边变量必须是 **reg** 类型
- **initial** 语句从0时刻开始执行且只执行一次
 - 如果有多个**initial**块，它们都从0时刻开始并行独立执行，独立完成执行。
- 如果在**initial**语句中有多条行为语句，那么需用 **begin/end** 组合在一起。

More on **initial** statements

- Initial statement very useful for testbenches
- Initial statements **don't** synthesize
- Don't use them in DUT (DUT: device under test)
Verilog (stuff you intend to synthesize)

initial Blocks

```
`timescale 1 ns / 100 fs
module full_adder_tb;
  reg [2:0] stim;
  wire s, c;

  add_full DUT (e, s, stim[2], stim[1], stim[0]); // instantiate DUT

  // monitor statement is special - only needs to be made once,
  initial $monitor("%t: s=%b c=%b stim=%b", $time, s, c, stim[2:0]);


  // tell our simulation when to stop
  initial #50 $stop;

  initial begin // stimulus generation
    for (stim = 3'h0; stim < 3'h8; stim = stim + 1) begin
      #5;
    end
  end
end
endmodule
```

all initial blocks start at time 0

*multi-statement block enclosed by **begin** and **end***

Another **initial** Statement Example

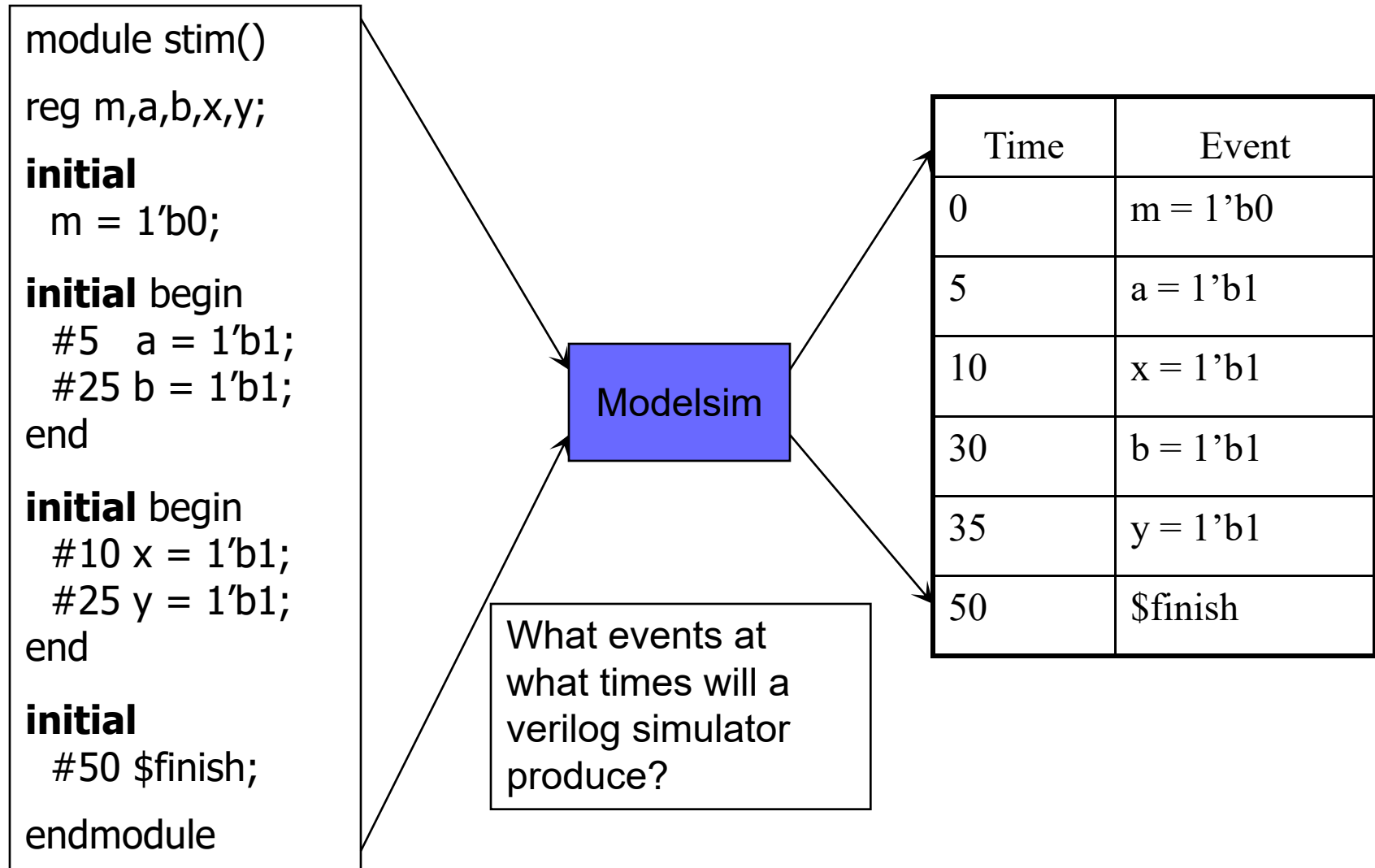

always statements

- **always**语句重复执行
 - 从0时刻开始不断循环执行;
 - 可以使用触发/敏感事件列表来控制操作; **@(a or b or c)**
 - 没有触发事件, 将在0时刻无限循环执行。

```
module clock_gen (output reg clock);  
  
initial  
    clock = 1'b0;                // must initialize in initial block  
  
always                // no trigger list for this always  
    #10 clock = ~clock;        // 带有时序控制  
                                //产生周期为20时间单位的波形  
  
endmodule
```

always的事件控制方式

- **always**是基于事件执行，有两种类型的事件控制方式
 - 边沿触发事件控制:用来描述时序逻辑电路
 - 电平敏感事件控制:用来描述组合逻辑电路
- **always @(posedge clk)** // clk从低电平->高（正沿）
 cur_state=next_state; // 就执行赋值语句
- **always @(negedge reset)** // reset从高->低（负沿）
 count=0; // 就执行赋值语句
- **always @ (posedge clear or negedge reset)**
 Q=0;
- 不可以同时包括同一个信号的上升沿和下降沿

电平敏感信号列表

- 只要列表内有信号发生电平变化，就执行该 **always** 结构中的内容。
- Original way to specify trigger list
always @ (X1 or X2 or X3)
- In Verilog 2001 can use , instead of **or**
always @ (X1, X2, X3)
- Verilog 2001 also has * for *combinational only*
always @ (*) //“*”代表所有输入信号，可防止遗漏
- 不可以同时包括电平敏感事件和边沿敏感事件

Some mixed simulation tools in use today still do not support Verilog 2001.

Example: 比较器

```
module compare_4bit_behave(output reg A_gt_B, A_lt_B, A_eq_B,  
                           input [3:0] A, B);
```

```
  always@( A or B) begin
```

```
    if ( A > B )
```

```
      { A_gt_B, A_lt_B, A_eq_B } = 3'b100;
```

```
    else if ( A == B)
```


```
      { A_gt_B, A_lt_B, A_eq_B } = 3'b001;
```

```
    else
```

```
      { A_gt_B, A_lt_B, A_eq_B } = 3'b010;
```

```
  end
```

```
endmodule
```

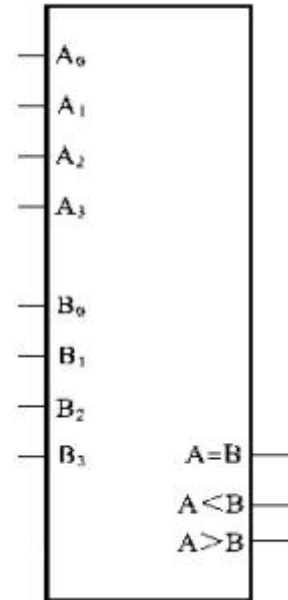

Flush out this template with sensitivity list and implementation
Hint: a if...else if...else statement is best for implementation

□ if-else 条件语句

```
if (条件表达式)      块语句1  
else if (条件表达式2) 块语句2  
.....  
else if (条件表达式n) 块语句n  
else                  块语句n+1
```

□ case 语句

```
case (敏感表达式)  
  值1:      块语句1  
  值2:      块语句2  
  .....  
  值n:      块语句n  
  default:  块语句n+1  
endcase
```

□ for循环语句

```
for (表达式1; 表达式2; 表达式3) 块语句
```

if...else if...else statement

- General forms...

```
If (condition) begin
    <statement1>;
    <statement2>;
end
```


Of course the compound statements formed with **begin/end** are optional.

```
If (condition)
begin
    <statement1>;
    <statement2>;
end
else
begin
    <statement3>;
    <statement4>;
end
```

```
If (condition)
begin
    <statement1>;
    <statement2>;
end
else if (condition2)
begin
    <statement3>;
    <statement4>;
end
else
begin
    <statement5>;
    <statement6>;
end
```

How does and if...else if...else statement synthesize?
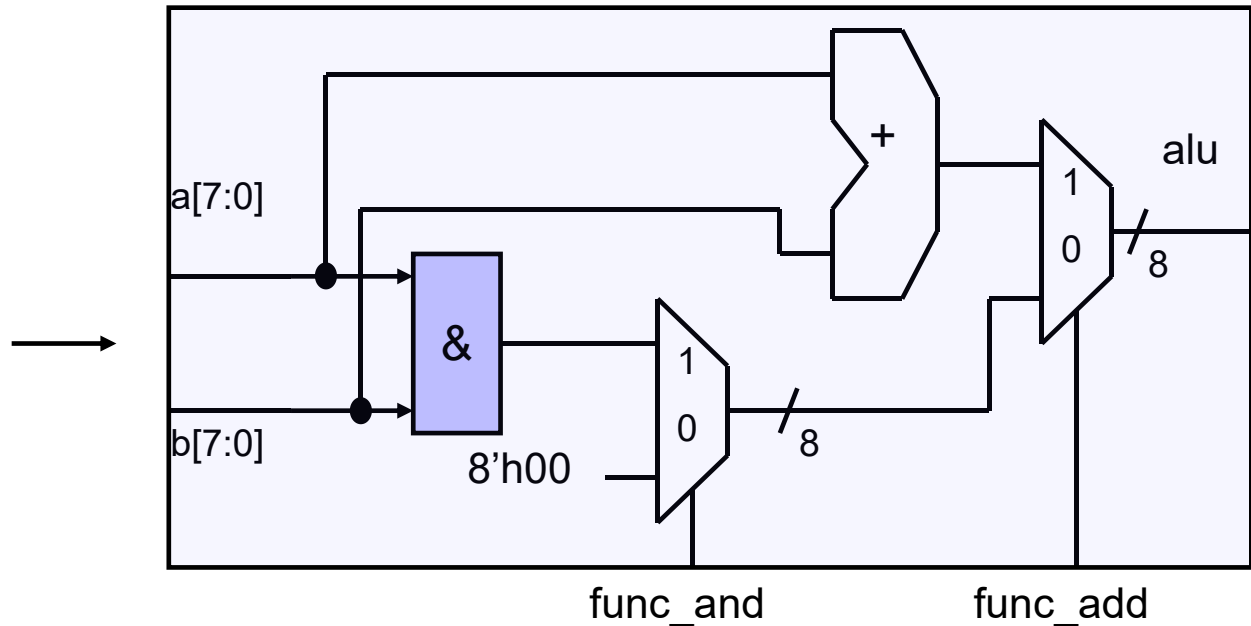
```
if (func_add)
    alu = a + b;
else if (func_and)
    alu = a & b;
else
    alu = 8'h00;
```




if statement synthesis (continued)

```
if (a)  
  func = c & d;  
else if (b)  
  func = c | d;
```

How does this
synthesize?

if 要加上else，以防
止锁存器的发生

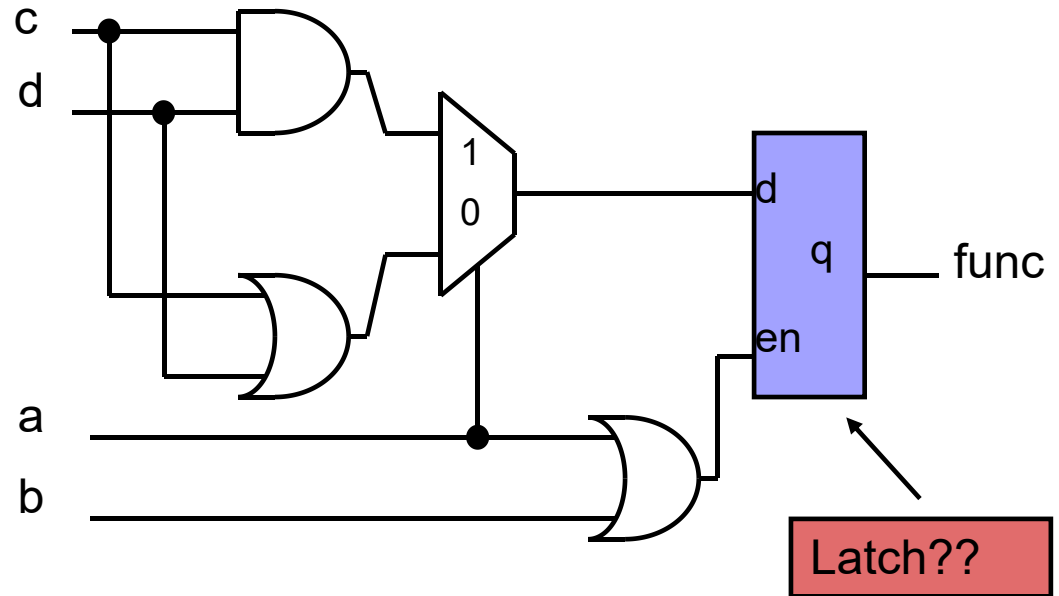

语句不完整即有某些情况的输入对输出无任何影响，根据锁存器的特征，反映到硬件电路即会产生锁存器。

More on **if** statements...

- Watch the sensitivity lists...what is missing in this example?

```
always @(a, b) begin  
    temp = a - b;  
    if ((temp < 8'b0) && abs)  
        out = -temp;  
    else out = temp;  
end
```

注意敏感信号的完备性：
必须将所有的输入信号和
条件判断信号都列在信号
列表中。

//带同步清0、同步置1的D触发器

```
always @ (posedge clk) begin  
    if (reset) q <= 0;  
    else if (set) q <= 1;  
    else q <= data;  
end
```

What is being coded here?

Is it synchronous or asynch?

Does the reset or the set have
higher priority?

Example: 7段数码管的显示译码器

```
module _7seg_display( in,SEG);
  input [3:0] in;    // 二进制输入
  output reg[7:0] SEG; // 7-seg display 输出。0--ON, 1--OFF
                      // 对应关系, SEG[0]->a,SEG[1]->b, ...
```

```
always@( in ) begin
```

```
  case (in[3:0])
```

```
    4'b0000 : SEG = 8'b11000000; // 0
    4'b0001 : SEG = 8'b11111001; // 1
    4'b0010 : SEG = 8'b10100100; // 2
    4'b0011 : SEG = 8'b10110000; // 3
    4'b0100 : SEG = 8'b10011001; // 4
    4'b0101 : SEG = 8'b10010010; // 5
    4'b0110 : SEG = 8'b10000010; // 6
    4'b0111 : SEG = 8'b11111000; // 7
    4'b1000 : SEG = 8'b10000000; // 8
    4'b1001 : SEG = 8'b10010000; // 9
    4'b1010 : SEG = 8'b10000110; // E
    default : SEG = 8'b11111111; // All OFF
```


```
  endcase
```

```
end
```

```
endmodule
```

h g f e d c b a

显示0: 1 1 0 0 0 0 0 0

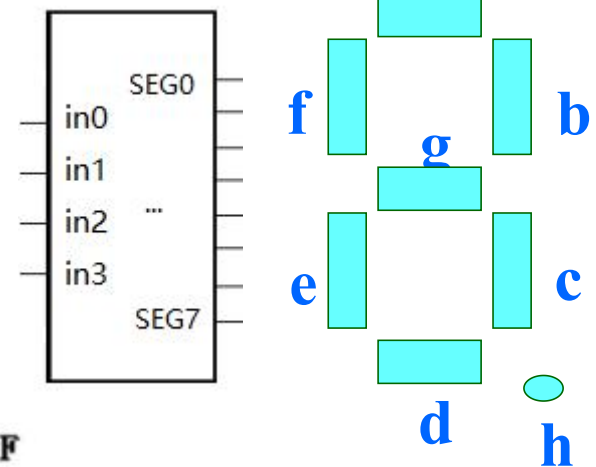

case Statements

- Verilog 有3种形式的case语句:
 - ⑩ **case**, **casex**, and **casez**
- 表达式按顺序与各分支项值按位匹配
 - 两者位宽相同!
- **case**: 是一种全等比较
 - Can detect **x** and **z** ! (good for testbenches)
- **casez**
 - 比较双方有一方的某些位的值是z, 那么这些位的比较就不予考虑, 而只关注其他位的比较结果
- **casex**
 - 比较双方有一方的某些位的值是x和z, 就不予考虑
- ? 可用来代替**z**, 表示无关位

```


if (func_add)
    alu = a + b;
else if (func_and)
    alu = a & b;
else alu = 8'h00;

```

```

case({func_add, func_and})
    2'b00: alu = 8'h00;
    2'b01: alu = a & b;
    2'b1x: alu = a + b;
    default: alu = 8'h00;
endcase

```

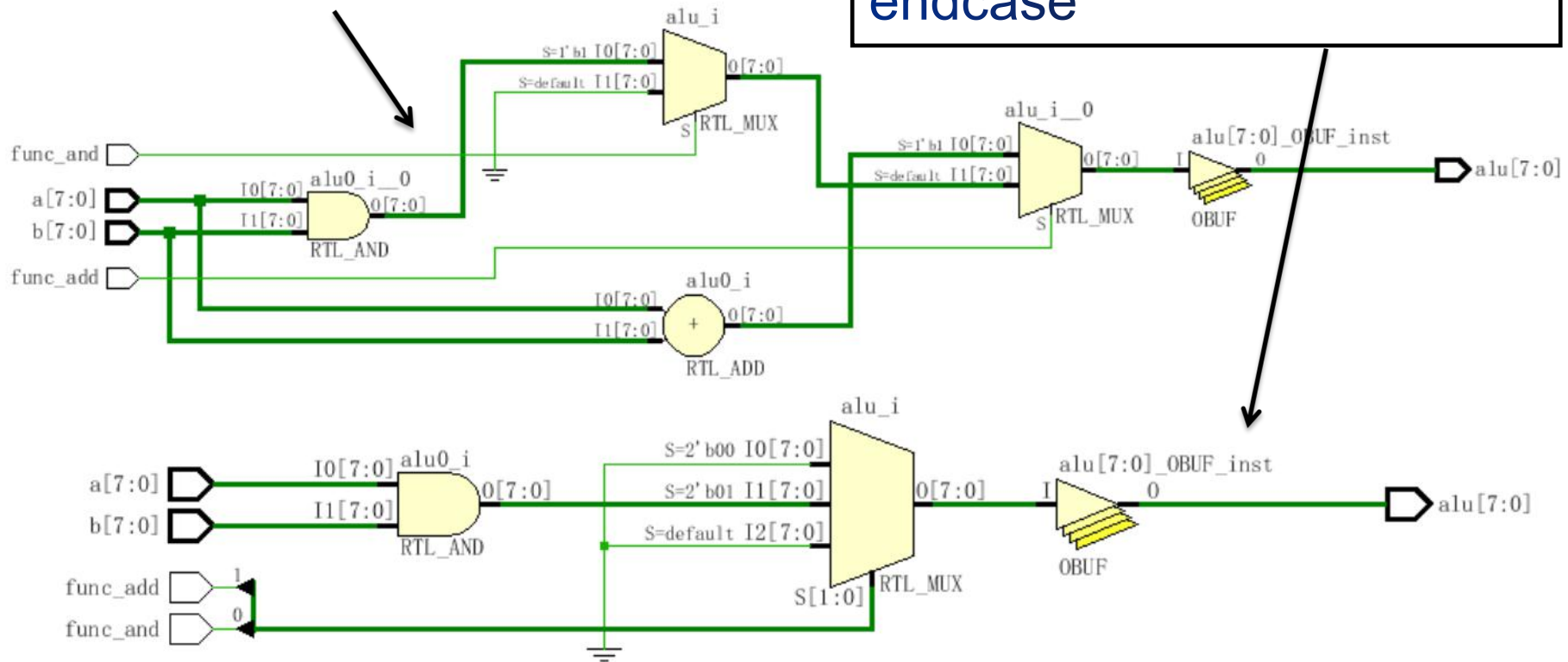

case的index列表里的x和z，都被综合工具认为是不可达状态,被去掉了。

Loops in Verilog

- We already saw the **for** loop:

```
reg [15:0] rf[0:15]; // memory structure for modeling register file
reg [5:0] w_addr;    // address to write to

for (w_addr=0; w_addr<16; w_addr=w_addr+1)
    rf[w_addr[3:0]] = 16'h0000;    // initialize register file memory
```

- There are 3 other loops available:
 - While loops
 - Repeat loop
 - Forever loop

while loops

- Executes until boolean condition is not true

⑩ If boolean expression false from beginning it will never execute loop

```
reg [15:0] flag;  
reg [4:0] index;  
  
initial begin // 找非0标志位  
    index=0;  
    found=1'b0;  
    while ((index<16) && (!found)) begin  
        if (flag[index]) found = 1'b1;  
        else index = index + 1;  
    end  
    if (!found) $display("non-zero flag bit not found!");  
    else $display("non-zero flag bit found in position %d",index);  
end
```

Handy for cases where
loop termination is a more
complex function.

Like a search

repeat Loop

- 执行指定的循环次数
 - ⑩ Repeat的循环次数可以是一个变量，但
 - ✓ 其值在开始循环时得到计算，从而得以事先确定循环次数
 - ✓ 如果其值在循环执行期间发生更改，也不会更改迭代次数
- 在testbench，常与 @(posedge clk) 事件控制一起使用，用来等待固定数量的时钟。

initial begin

```
inc_DAC = 1'b1;           // 等待clk的4095个正沿
repeat(4095) @(posedge clk); // bring DAC right up to point of rollover
inc_DAC = 1'b0;
inc_smpl = 1'b1;
repeat(7)@(posedge clk);    // bring sample count up to 7
inc_smpl = 1'b0;
```

end

forever loops

- 无限循环。常用于产生周期性的波形，用来作为仿真测试信号。它与**always**的不同之处是不能独立在程序中，必须写在**initial**块中
- Only a **\$stop**, **\$finish** or a specific **disable** can end a **forever** loop.

```
initial begin  
    clk = 0;  
    forever    //每隔10个时间单位clk反相一次  
        #10 clk = ~ clk;  
end
```

Clock generator is by far the most common use of a forever loop

// 4b乘法器, $R=A*B$

module mult4b(output reg [7:0] R, input [3:0] A, input [3:0] B);

integer i;

always @(A, B) **begin**

R = 0;

for(i=0; i<=3; i=i+1)


if(B[i]) R = R + (A<<i);

end

endmodule

A:	1101
B:	1011
*	-----
	1101
	1101
	1101

+	-----
	10001111

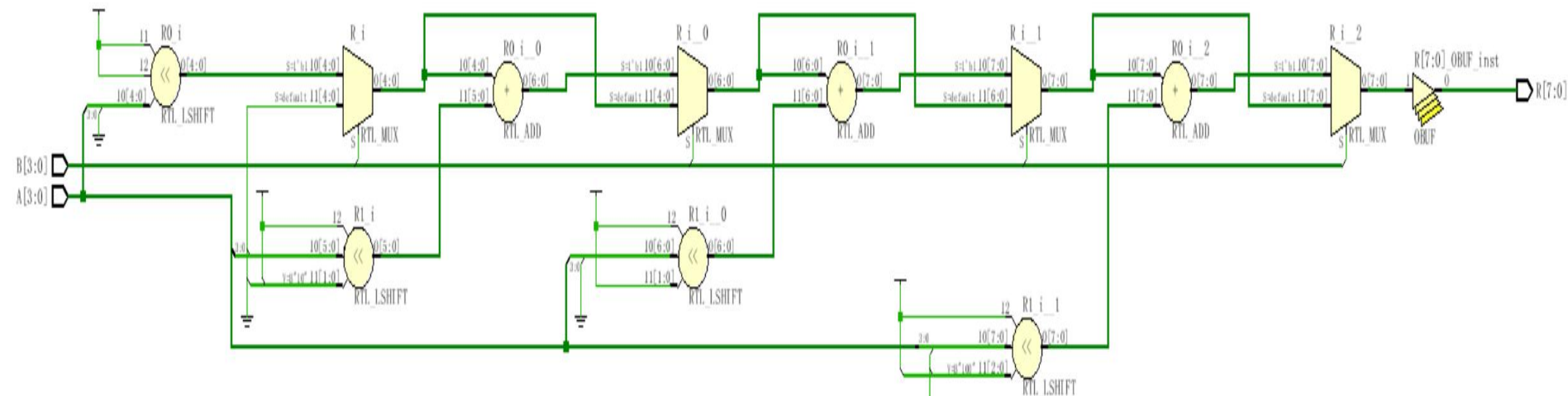

HDL里的for是并行展开，代码看似简洁，电路规模扩大了n倍。

过程赋值语句

❑ 阻塞型过程赋值：=

前一条语句没有完成赋值过程之前，后面的语句不能被执行

❑ 非阻塞型过程赋值：<=

一条非阻塞赋值语句的执行，不会影响块中其它语句的执行

基本形式： <寄存器变量>=<表达式>;

外部模式： <定时控制> <寄存器变量>=<表达式>; //定时满足，RHS被计算和赋值

内部模式： <寄存器变量>= <定时控制> <表达式>; //计算RHS，定时满足后再赋值


定时控制分为两类： 延时控制 #delay

事件控制 @(事件控制敏感表)

阻塞性赋值

- 当前的赋值语句阻断了其后的语句，即后面的语句必须等到当前的赋值语句执行完毕才能执行
- Works a lot like software (**danger!**)
- 用于组合逻辑

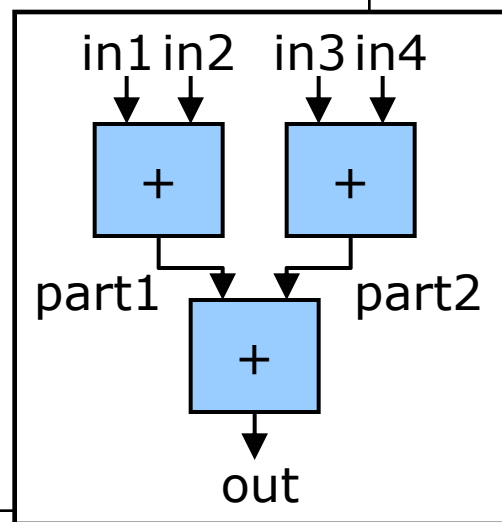
```
module addtree(output reg [9:0] out,  
               input [7:0] in1, in2, in3, in4);  
  
reg [8:0] part1, part2;  
always @(in1, in2, in3, in4) begin  
    part1 = in1 + in2;  
    part2 = in3 + in4;  
    out = part1 + part2;  
  
end  
endmodule
```



非阻塞性赋值

- 如果没有定时控制，则同时计算RHS和更新LHS
- 用于时序逻辑
- 只能用在"initial"和"always"中
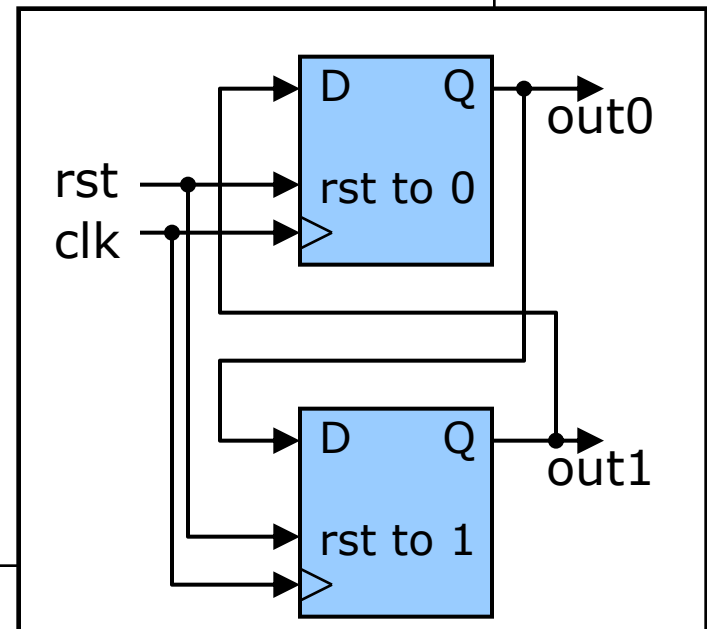
```
module swap(output reg out0, out1, input rst, clk);  
  always @(posedge clk) begin  
    if (rst) begin  
      out0 <= 1'b0;  
      out1 <= 1'b1;  
    end  
    else begin  
      out0 <= out1;  
      out1 <= out0;  
    end  
  end  
endmodule
```



Swapping if done in Blocking

- In blocking, need a “temp” variable

```
module swap(output reg out0, out1, input in0, in1, swap);
```

```
reg temp;
```

```
always @(*) begin
```

```
    out0 = in0;
```

```
    out1 = in1;
```

```
    if (swap) begin
```

```
        temp = out0;
```


```
        out0 = out1;
```

```
        out1 = temp;
```

```
    end
```

```
end
```


```
endmodule
```

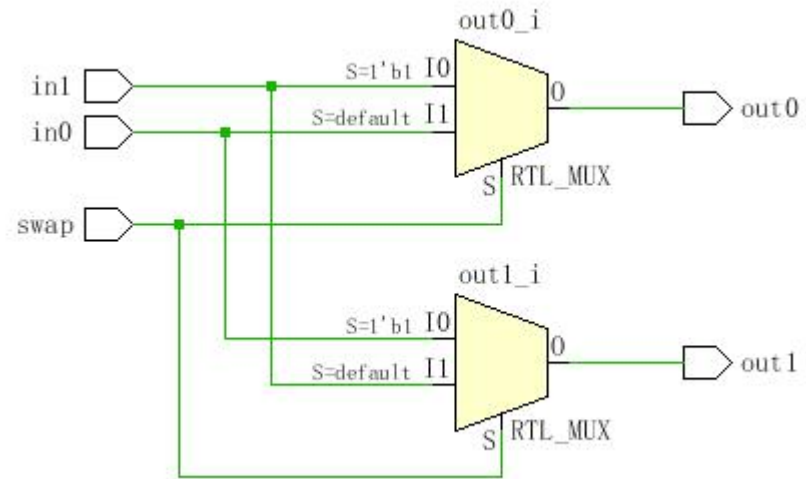

Which values get included on the sensitivity list from *?

Swapping if done in Non-Blocking

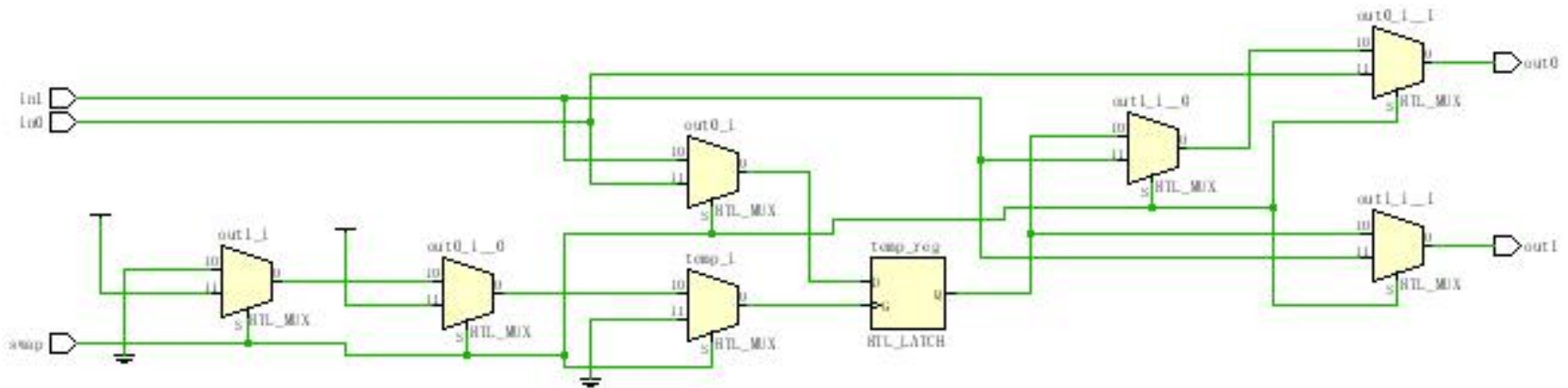
```
module swap(output reg out0, out1, input in0, in1, swap);  
  reg temp;  
  always @(*) begin  
    out0 <= in0;  
    out1 <= in1;  
    if (swap) begin  
      temp <= out0;  
      out0 <= out1;  
      out1 <= temp;  
    end  
  end  
endmodule
```



More on Blocking

- Called blocking because....
 - ⑩ The evaluation of subsequent statements <RHS> are **blocked**, until the <LHS> assignment of the current statement is completed.
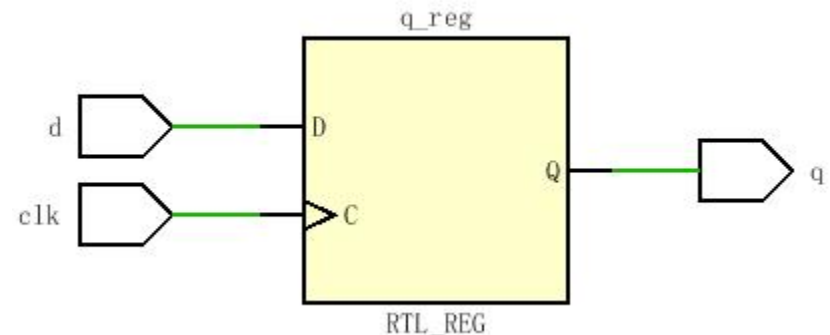
```
module pipe(clk, d, q);  
input clk,d;  
output q;  
reg q,q1,q2;  
always @(posedge clk) begin  
    q1 = d;  
    q2 = q1;  
    q  = q2;  
end //在一个时钟沿，d传递到q  
endmodule
```



More on Non-Blocking

- With non-blocking statements the <RHS> of subsequent statements are not blocked. They are all evaluated simultaneously.

```
module pipe(clk, d, q);
```

```
input clk,d;
```

```
output q;
```

```
reg q,q1,q2;
```

```
always @(posedge clk) begin
```


```
    q1 <= d;
```

```
    q2 <= q1;
```

```
    q <= q2;
```

```
end //d传递到q需要间隔三个时钟
```

```
endmodule;
```

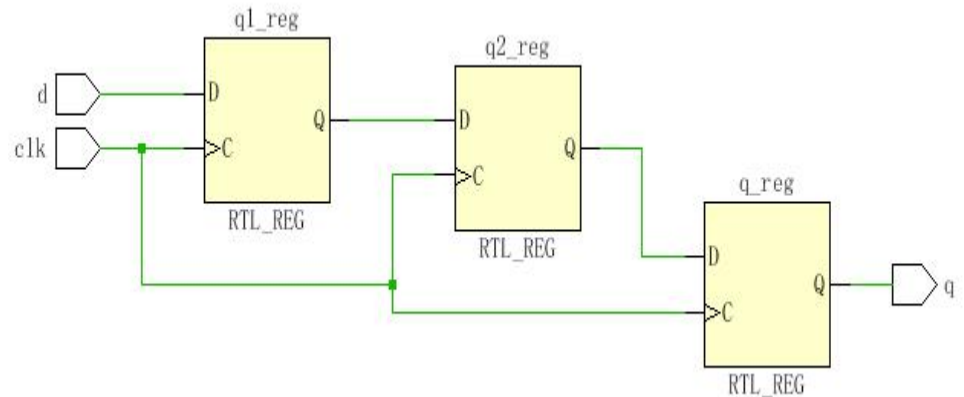

So Blocking is no good and we should always use Non-Blocking??

- Consider combinational logic

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

Does this work?

The inputs (a,b,c,d) in the sensitivity list change, and the always block is evaluated.

New assignments are scheduled for tmp1 & tmp2 variables.

A new assignment is scheduled for z using the **previous** tmp1 & tmp2 values.

Why not non-Blocking for Combinational

- Can we make this example work?

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

Yes

Put tmp1
& tmp2 in
the
trigger
list

```
module ao4(z,a,b,c,d);  
input a,b,c,d;  
output z;  
reg z,tmp1,tmp2;  
always @(a,b,c,d,tmp1,tmp2) begin  
    tmp1 <= a & b;  
    tmp2 <= c & d;  
    z <= tmp1 | tmp2;  
end  
endmodule
```

What is the downside of this?

任务(task)和 函数(function)

```
module Name (port list) ;
```

```
.....
```

```
task 任务名;  
    参数与类型说明;  
    局部变量说明; //静态的  
    过程语句  
endtask
```

```
function <位宽说明> 函数名;  
    输入参数与类型说明;  
    局部变量说明; //静态的  
    过程语句  
endfunction
```

```
endmodule
```

可以在模块不同位置执行共同代码

任务(task)和 函数(function)

❑ 差异

- 任务可以含有**时序控制**，而函数则没有；
- 任务可以有**输入和输出参数**，而函数至少一个输入参数，没有输出参数；
- 任务的调用是通过**调用语句**，而函数调用出现在**表达式**中。

functions

- 函数的定义和调用都包括在一个module内
 - 函数调用在表达式中 (RHS)
- 用于实现组合逻辑
 - 不能包含任何时延、时序、事件控制
 - 可以调用其他函数，不能调用任务
 - 只使用阻塞赋值，行为语句
- 输入/输出
 - 至少一个输入参数，不能有输出或者双向(inout)参数
 - 返回一个值，与函数同名的寄存器变量在函数中被隐式地声明，通过对该寄存器赋值来返回函数值，可以指定返回值的宽度 (缺省1-bit)

Function Example

```
module arithmetic_unit (result_1, result_2, operand_1, operand_2,);
```

```
  output          [4: 0] result_1;
```

```
  output          [3: 0] result_2;
```

```
  input           [3: 0] operand_1, operand_2;
```

```
  assign result_1 = sum_of_operands (operand_1, operand_2);
```

```
  assign result_2 = larger_operand (operand_1, operand_2);
```

function call



```
function [4: 0] sum_of_operands(input [3:0] operand_1, operand_2);
```

```
  sum_of_operands = operand_1 + operand_2;
```

```
endfunction
```

function output



function inputs




```
function [3: 0] larger_operand(input [3:0] operand_1, operand_2);
```

```
  larger_operand = (operand_1 >= operand_2) ? operand_1 : operand_2;
```

```
endfunction
```

```
endmodule
```

Function Example

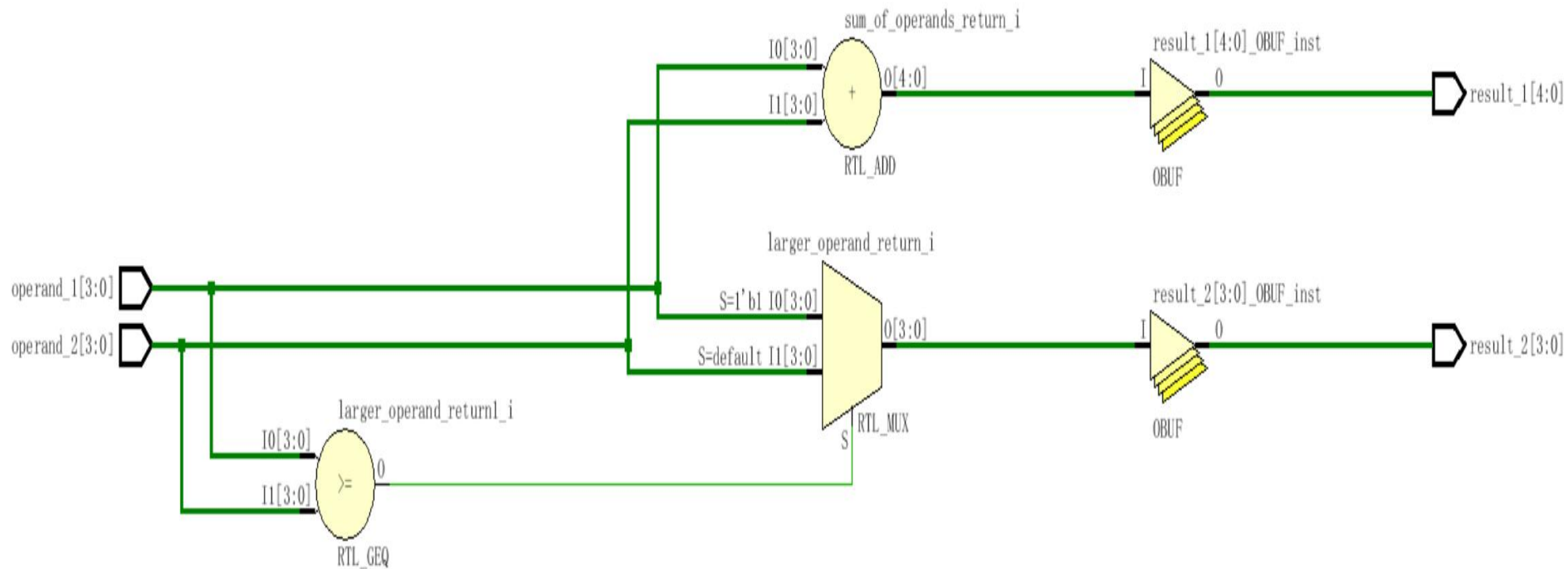

tasks (much more useful than functions)

Functions	Tasks
函数只能调用其他函数，不能调用任务	任务可以调用其他任务和函数
函数不能包含任何延迟，事件或者时序控制	任务可以包含延迟，事件或者时序控制 (i.e. ➔ @, #)
函数至少要有有一个输入参数，也可以有多个输入参数	任务可以没有或者有多个输入，输出，双向参数
函数只能返回一个值，不能有输出或者双向参数	任务不返回任何值，但是返回多个输出或双向参数值

Why use Tasks?

- 把大程序分成小程序
- 在测试台上使用任务非常方便
 - 将常见的测试例程分解为任务
 - ✓ 初始化任务
 - ✓ 激励信号产生任务
 - ✓ 自检任务
 - 顶层测试主要是对任务的调用

Task Example [Part 1]

```
module adder_task (c_out, sum,  
  output reg    [3: 0]  sum;  
  output reg    c_out;  
  input [3: 0]  data_a, data_b;  
  input        clk, reset, c_in;
```

任务调用:

- (1) 任务调用语句是过程性语句, 只能出现在**always** 语句或**initial** 语句中;
- (2) 任务调用语句中的参数列表顺序和类型必须和任务定义中的一致;
- (3) 输出参数必须是寄存器类型。

```
always @(posedge clk or posedge reset) begin
```

```
  if (reset) {c_out, sum} <= 0;
```

```
  else add_values (sum, c_out, data_a, data_b, c_in); //任务调用
```

```
end
```

```
// Continued on next slide
```

Task Example

任务定义:

- (1) 任务的参数不受限制
- (2) 在任务中可以调用其他的任务或函数。
- (3) 任务定义内不能出现 **initial** 和 **always** 过程块。

// Continued from previous

task add_values;

output reg [3: 0] SUM;

output reg C_OUT;

input [3: 0] DATA_A, DATA_B;

input C_IN;

{C_OUT, SUM} = DATA_A + (DATA_B + C_IN);

endtask

endmodule


} **task outputs**

} **task inputs**

- Could have instead specified inputs/outputs using a port list.

task add_values (**output reg** [3: 0] SUM, **output reg** C_OUT,
 input [3:0] DATA_A, DATA_B, **input** C_IN);

Task Example [Part 3]

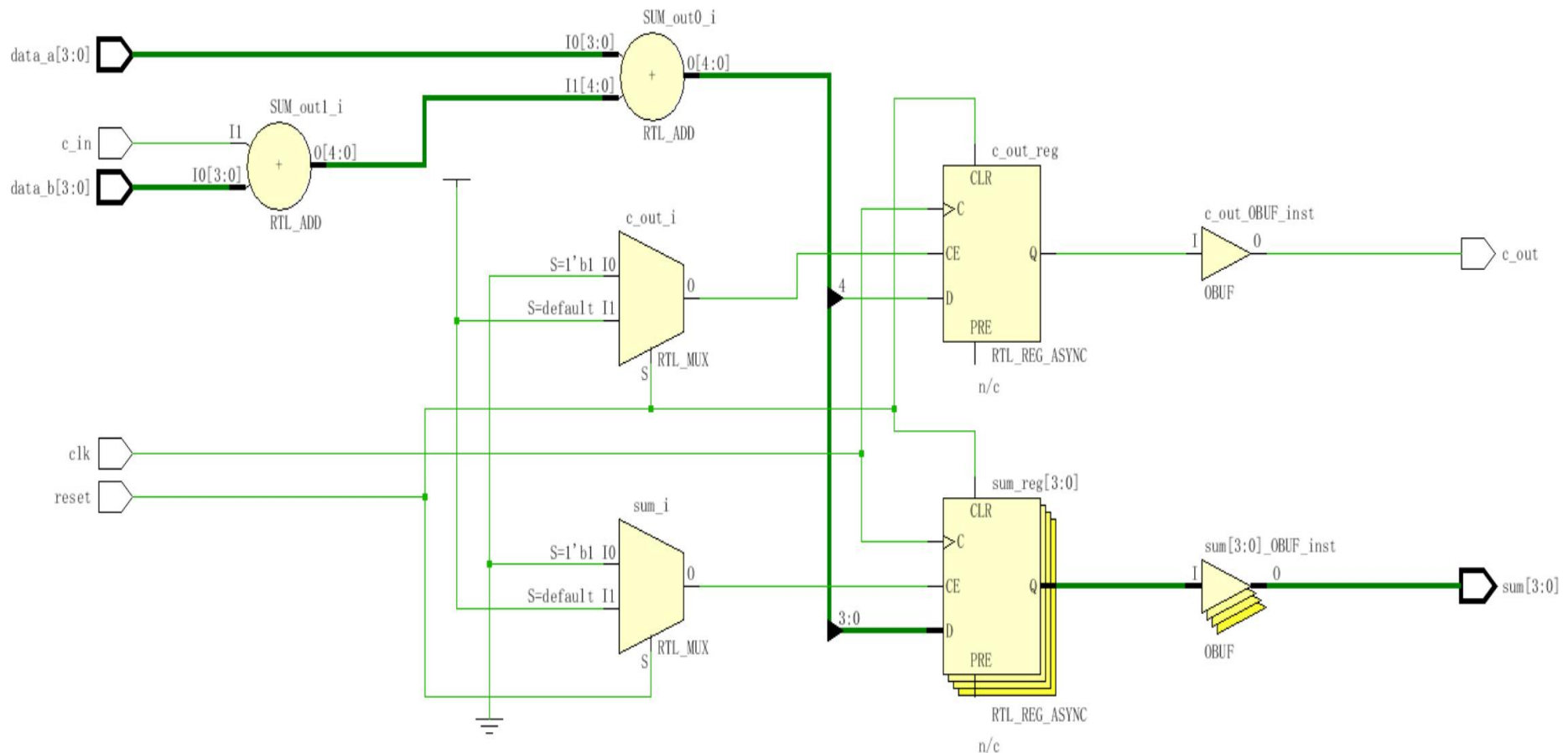

时序控制

- “#”符号引入的延迟控制，时间的长度由<time>值确定。

```
# <time> <statement> ;
```

- “@”符号引入的事件控制

```
@ (<posedge>|<negedge>|<signals> ) <statement>;
```

- 等待语句。表达式为真之前，延时下一个语句的执行。

```
wait (<expression>) <statement> ;
```

- 延迟定义块。对模块中某一指定的路径进行延迟定义，这一路径连接模块的输入端口与输出端口（或双向端口）。

```
specify  
    (<expression>) = <time>;  
    .....  
endspecify
```

```
(a=>out)=9;
```

```
//从输入a到out的每位延迟为9
```


命名程序块

- Blocks (begin/end) or (fork/join) can be named
 - 命名块中可以声明局部变量;
 - 命名块中声明的变量可以通过层次名引用进行访问;
 - 命名块可以被禁用 (例如停止其执行)

```
module top();  
    initial begin: block1 //名字为block1的过程命名块  
        integer i;        // i 是block1命名块的静态局部变量  
        ...               //可以用层次名top.block1.i 被其他模块访问  
    end                    // end of block1  
endmodule
```

disable Statement

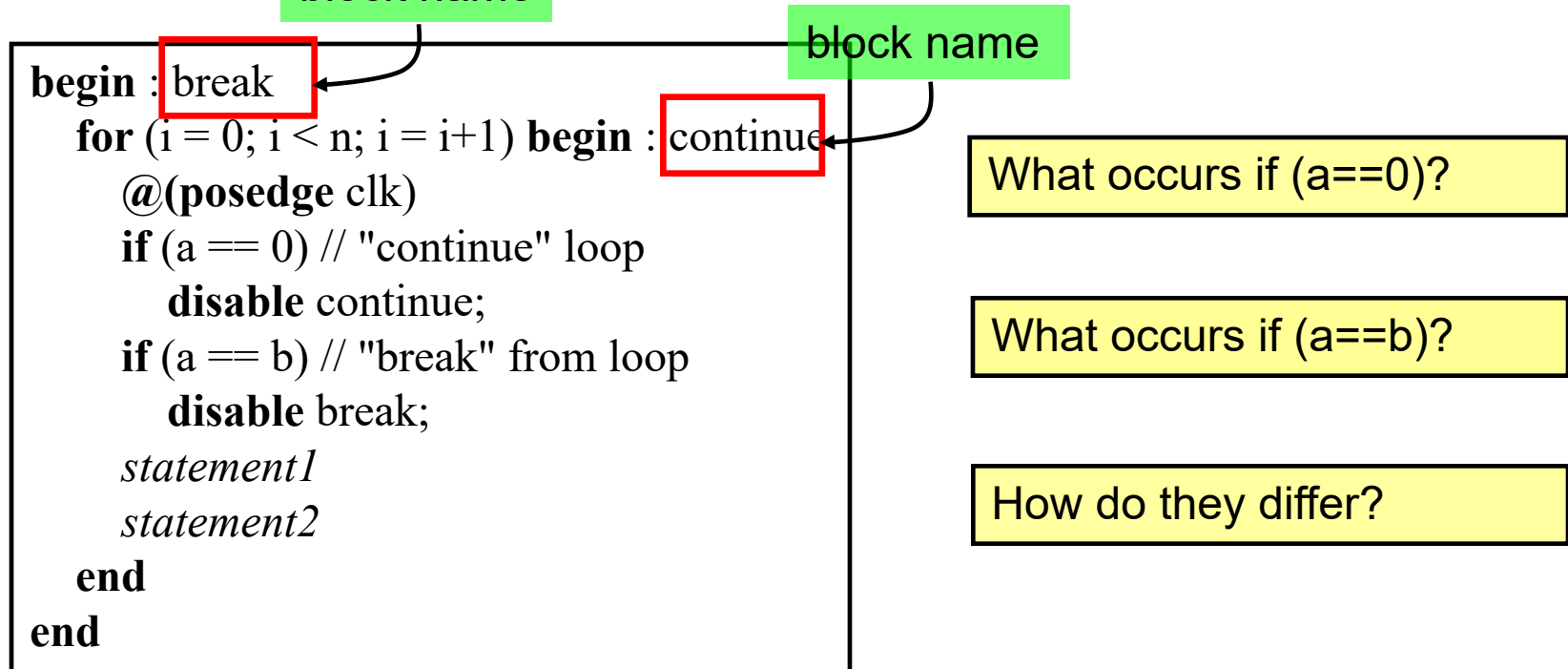- Similar to the “break” statement in C
 - Disables execution of the current block (not permanently)



File I/O

- If we don't want to hard-code all information in the testbench, we can use input files
- Help automate testing
 - One file with inputs
 - One file with expected outputs
- Can have a software program generate data
 - Create the inputs for testing
 - Create “correct” output values for testing
 - Can use files to “connect” hardware/software system

Opening/Closing Files

- **\$fopen** opens a file and returns an integer descriptor
 - integer fd = \$fopen(“filename”);**
 - integer fd = \$fopen(“filename”, r);**
 - If file cannot be open, returns a 0
 - Can output to more than one file simultaneously by writing to the OR (|) of the relevant file descriptors
 - ✓ Easier to have “summary” and “detailed” results
- **\$fclose** closes the file
 - \$fclose(fd);**

Writing To Files

- Output statements have file equivalents
 - ✓ **\$fmonitor()**
 - ✓ **\$fdisplay()**
 - ✓ **\$fstrobe()**
 - ✓ **\$fwrite()** // write is like a display without the \n
- These system calls take the file descriptor as the first argument
 - ✓ **\$fdisplay(fd, “out=%b in=%b”, out, in);**

Reading From Files

- Read a binary file: **\$fread**(destination, fd);
 - Can specify start address & number of locations too
 - Good luck! I have never used this.
- Very rich file manipulation (see IEEE Standard)
 - ✓ \$fseek(), \$fflush(), \$ftell(), \$rewind(), ...
- Will cover a few of the more common read commands next

Using **\$fgetc** to read characters

```
module file_read()
parameter EOF = -1;
integer file_handle,error,indx;
reg signed [15:0] wide_char;
reg [7:0] mem[0:255];
reg [639:0] err_str;

initial begin
  indx=0;
  file_handle = $fopen("text.txt","r");
  error = $ferror(file_handle,err_str);
  if (error==0) begin
    wide_char = 16'h0000;
    while (wide_char!=EOF) begin
      wide_char = $fgetc(file_handle);
      mem[indx] = wide_char[7:0];
      $write("%c",mem[indx]);
```

```
      indx = indx + 1;
    end
  end
  else $display("Can't open file...");
  $fclose(file_handle);
end
endmodule
```

The quick brown fox jumped
over the lazy dogs

text.txt

When finished the array *mem* will contain the characters of this file one by one, and the file will have been echoed to the screen.

Why wide_char[15:0] and why signed?

Using **\$fgets** to read lines

```
module file_read2()

integer file_handle,error,indx,num_bytes_in_line;
reg [256*8:1] mem[0:255],line_buffer;
reg [639:0] err_str;

initial begin
    indx=0;
    file_handle = $fopen("text2.txt","r");
    error = $ferror(file_handle,err_str);
    if (error==0) begin
        num_bytes_in_line = $fgets(line_buffer,file_handle);
        while (num_bytes_in_line>0) begin
            mem[indx] = line_buffer;
            $write("%s",mem[indx]);
            indx = indx + 1;
            num_bytes_in_line = $fgets(line_buffer,file_handle);
        end
    end
    else $display("Could not open file text2.txt");
```

\$fgets() returns the number of bytes in the line. When this is a zero you know you hit EOF.

Using **\$fscanf** to read files

```
module file_read3()
integer file_handle,error,indx,num_matches;
reg [15:0] mem[0:255][1:0];
reg [639:0] err_str;

initial begin
    indx=0;
    file_handle = $fopen("text3.txt","r");
    error = $ferror(file_handle,err_str);
    if (error==0) begin
        num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
        while (num_matches>0) begin
            $display("data is: %h %h",mem[indx][0],mem[indx][1]);
            indx = indx + 1;
            num_matches = $fscanf(file_handle,"%h %h",mem[indx][0],mem[indx][1]);
        end
    end
    else $display("Could not open file text3.txt");
```

12f3	13f3
abcd	1234
3214	21ab

<i>text3.txt</i>

Loading Memory Data From Files

- This is very useful (memory modeling & testbenches)
 - **\$readmemb**("<file_name>",<memory>);
 - **\$readmemb**("<file_name>",<memory>,<start_addr>,<finish_addr>);
 - **\$readmemh**("<file_name>",<memory>);
 - **\$readmemh**("<file_name>",<memory>,<start_addr>,<finish_addr>);
- **\$readmemh** → Hex data...**\$readmemb** → binary data
 - But they are reading ASCII files either way (just how numbers are represented)

// addr data @0000 10100010 @0001 10111001 @0002 00100011
example "binary" file

// addr data @0000 A2 @0001 B9 @0002 23
example "hex" file

//data A2 B9 23
address is optional for the lazy

Example of \$readmemh

```
module rom(input clk; input [7:0] addr; output [15:0] dout);
```

```
reg [15:0] mem[0:255];    // 16-bit wide 256 entry ROM
```

```
reg [15:0] dout;
```

```
initial
```

```
    $readmemh("constants",mem);
```

```
always @(negedge clk) begin
```

```
    //////////////////////////////////////////////////////////////////
```


```
    // ROM presents data on clock low //
```

```
    //////////////////////////////////////////////////////////////////
```

```
    dout <= mem[addr];
```

```
end
```

```
endmodule
```

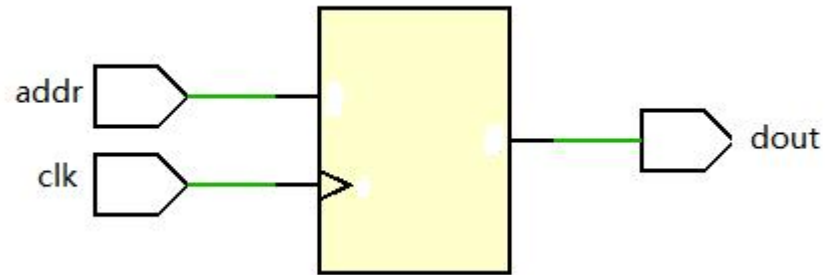

‘Include Compiler Directives

- **`include** filename

- Inserts entire contents of another file at compilation
- Can be placed anywhere in Verilog source
- Can provide either relative or absolute path names

- Example 1:

```
module use_adder8(...);
```

```
  `include "adder8.v" // include the task for adder8
```

- Example 2:

```
module cppc_dig_tb();
```

```
  `include "/home/ehoffman/ece551/project/tb_tasks.v"
```

- Useful for including tasks and functions in multiple modules